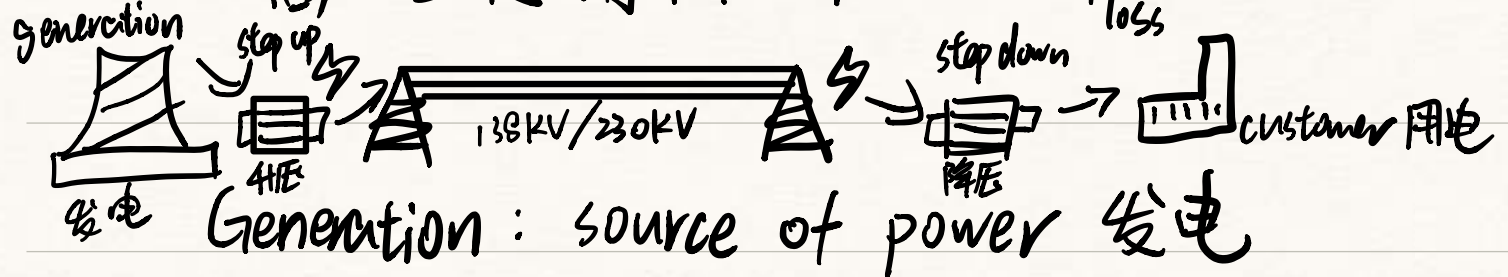



书 << Power System Analysis and Design >>

高电压传输 降低损耗 $P_{loss} \propto i^2 R$



Load: consumes power 负载

Transmission system: transmits power 传输

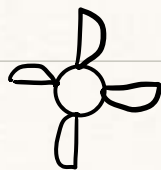 Turbine 涡轮机

{ Gas combustion 内燃 CT
steam 蒸气 ST
combined cycle 组合循环 CCT

可再生能源 renewable energy

Solar 太阳 { photovoltaic 光伏
Thermal 热
Concentrated 浓缩

(turbine 涡轮

Wind $\times$ $\rightarrow$ AC power { gear box 变速箱
power electronic converters AD转换

Geothermal Power 地热能

Tidal Power 潮汐能

Biomass 生物质能

Power (watts) 瓦特

K 10^3
M 10^6
G 10^9

$$P(t) = V(t) \cdot i(t)$$

Energy (Joules) 焦耳

$$1 \text{ J} = 1 \text{ W} \cdot \text{second (s)}$$

$$1 \text{ kWh} = 3.6 \times 10^6 \text{ J} \text{ 千瓦时}$$

$$1 \text{ Btu (British Thermal Unit)} = 1055 \text{ J} \text{ 英热}$$

$$1 \text{ MBtu} = 0.292 \text{ MWh}$$


电力系统 { AC/DC 交直流

60Hz 美 50Hz 其它

220V 中 380V 工业 110V 英美加...


以上内容了解即可

平均值 Average

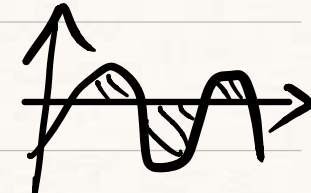AC交流 $V_{avg} = \frac{1}{T} \int_0^T v(t) dt = 0$ 


三相电压 Three phase power system

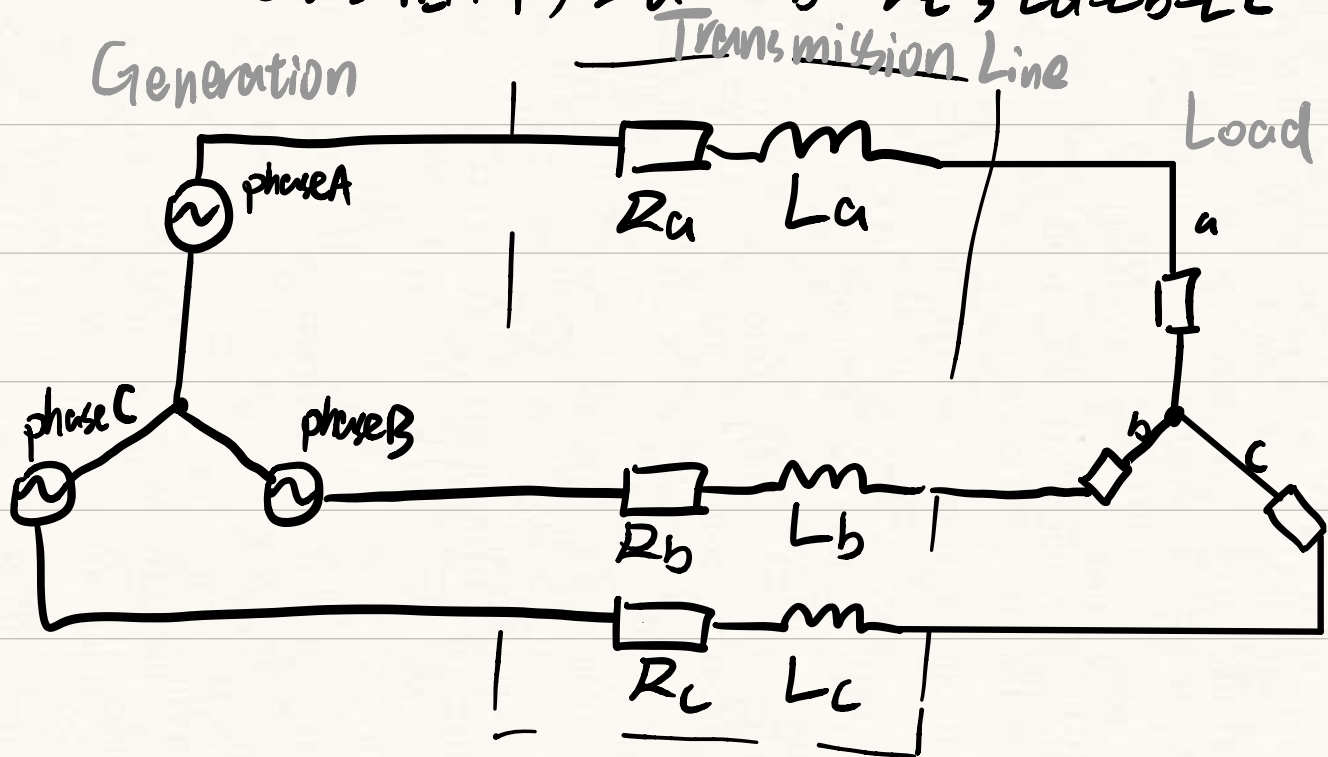3路相同, $R_a = R_b = R_c$, $L_a = L_b = L_c$



V & i are 3 phase balanced
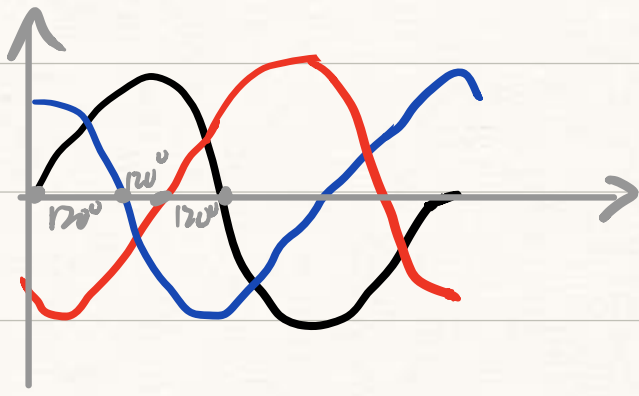
$$P_{total} = P_a + P_b + P_c = 3P_c \text{ 不变量 Constant}$$



定义 $i_a(t) = A \sin(\omega t)$

$i_b(t) = A \sin(\omega t - 120^\circ)$

$i_c(t) = A \sin(\omega t + 120^\circ)$

instantaneous value 瞬时值 V_{max}

Root mean square 有效值, 均方根

$V_{rms} = \sqrt{\frac{1}{T} \int_0^T v^2 dt}$, $v = V_{max} \cos \omega t$ ω 角频率 angular frequency

$$= \sqrt{\frac{V_{max}^2}{T} \int_0^T \cos^2 \omega t dt} = \frac{V_{max}}{\sqrt{T}}$$

$$\sqrt{\int_0^T \frac{\cos^2 \omega t + 1}{2} dt} = \sqrt{\int_0^T \frac{\cos 2\omega t}{2} dt + \int_0^T \frac{1}{2} dt}$$

$$= \sqrt{\left. \frac{\sin 2\omega t}{4\omega} \right|_0^T + \left. \frac{1}{2} t \right|_0^T} = \sqrt{\frac{\sin 2\omega T}{4\omega} + \frac{T}{2}}$$

$$= \frac{V_{max}}{\sqrt{T}} \cdot \frac{\sqrt{T}}{\sqrt{2}} = \frac{V_{max}}{\sqrt{2}}$$

欧拉公式 Euler's identity 共轭 conjugate

$$e^{j\theta} = \cos\theta + j\sin\theta$$

直角坐标

$$z = a + bj = \mu e^{j\theta}$$

$$z^* = a - bj = \mu e^{-j\theta}$$

$$A \cos(\omega t + \theta) = \frac{A}{\sqrt{2}} e^{j\theta} = \frac{A}{\sqrt{2}} \angle \theta$$

相乘 向量解相加
 $z_1 \cdot z_2 = \mu_1 \mu_2 \cdot e^{j(\theta_1 + \theta_2)}$
相除 向量解相减
 $\frac{z_1}{z_2} = \frac{\mu_1}{\mu_2} \cdot e^{j(\theta_1 - \theta_2)}$

$$US \text{ 频率 } f = 60 \text{ Hz}$$

$$CN \text{ 频率 } f = 50 \text{ Hz}$$

$$\omega = 2\pi f = 377 \text{ rad/s}$$

电阻 Resistor $V = RI$

电感 Inductor $V = j\omega LI$

电容 Capacity $V = \frac{1}{j\omega}$

阻抗 Impedance R, L, C 的总称 $Z = (R) + j(\omega L) - j(\omega C)$

导纳 Admittance 阻抗的倒数 $Y = \frac{1}{Z}$ 单位 Siemens (西门子)

Capacitor 设 $V(t) = V_{\max} \cos(\omega t + \theta)$

在电容线路中, $i(t) = C \frac{dV(t)}{dt} = C \cdot \omega \cdot V_{\max} \cdot \{-\sin(\omega t + \theta)\}$
 $= C \omega V_{\max} \cos(\omega t + \theta + 90^\circ)$

$$Z_C = \frac{V(t)}{i(t)} = \frac{\frac{V_{\max}}{\sqrt{2}} \angle \theta}{C \omega \frac{V_{\max}}{\sqrt{2}} \angle \theta + 90^\circ} = \frac{1}{C \omega} \angle -90^\circ = \frac{1}{j\omega C}$$

i 相位比 V 快 90°

current phasor leads the voltage by 90°

Indicator 设 $i(t) = I_{\max} \cos(\omega t + \theta)$

在电感电路中 $V(t) = L \frac{di(t)}{dt} = L \omega I_{\max} \cdot \{-\sin(\omega t + \theta)\}$
 $= L \omega I_{\max} \cos(\omega t + \theta + 90^\circ)$

$$Z_L = \frac{V(t)}{i(t)} = \frac{\frac{L \omega I_{\max}}{\sqrt{2}} \angle \theta + 90^\circ}{\frac{I_{\max}}{\sqrt{2}} \angle \theta} = L \omega \angle 90^\circ = j\omega L$$


i 相位比 V 慢 90°

current phasor lags the voltage by 90°

基尔霍夫定律 Kirchhoffs Circuit Law

KCL: 结点电流之和 (进, 出) 为零

KVL: 闭路电压之和为零

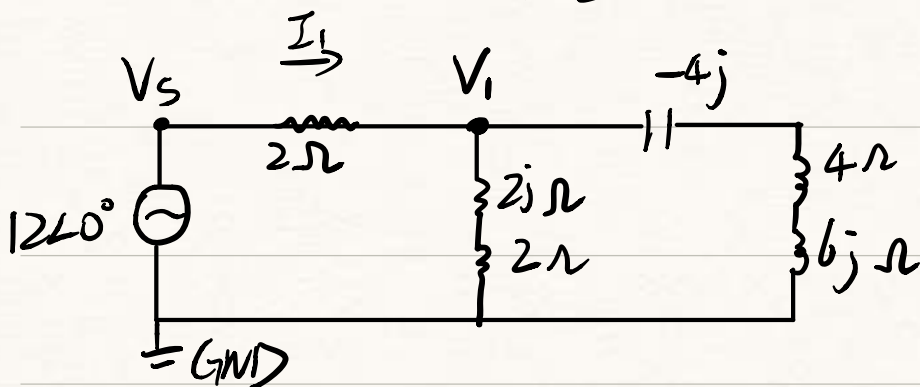

$$\text{KCL: } \frac{V_1 - V_s}{2} + \frac{V_1 - 0}{2 + 2j} + \frac{V_1 - 0}{4 + 6j - 4j} = 0$$

$$\Rightarrow V_1 \left[\frac{1}{2} + \frac{1}{2 + 2j} + \frac{1}{4 + 6j - 4j} \right] = \frac{V_s}{2} \quad (V_s = 12\angle 0^\circ)$$

$$\Rightarrow V_1 = 5.93\angle 20.2^\circ \text{ (V)}$$

功率 Power

$$\begin{aligned} \text{电阻 Resist } P(t) &= V(t) \cdot i(t) = V_{\max} I_{\max} \cos^2(\omega t + \theta) \text{ W} \\ &= \frac{1}{2} V_{\max} I_{\max} [1 + \cos(2\omega t + 2\theta)] \text{ W} \\ &= \frac{1}{2} \cdot \frac{V_{\max}^2}{R} [1 + \cos(2\omega t + 2\theta)] \text{ W} \end{aligned}$$

$$V = \frac{V_{\max}}{\sqrt{2}} \Rightarrow \frac{V^2}{R} + \frac{V^2}{R} \cos(2\omega t + 2\theta) \quad \checkmark$$

Indicator power $p(t) = V_{\max} \cos(\omega t + \theta) I_{\max} \cos(\omega t + \theta - 90^\circ)$
 $= \frac{1}{\omega L} V^2 \sin(2\omega t + 2\theta)$

Capacitor power $p(t) = \omega C V^2 \sin(2\omega t + 2\theta)$

电感电容两倍频率
 $\omega_L, \omega_C = 2\omega$

RLC电路中

$$\theta = \theta_V - \theta_I$$

real 实
 average power 平均功率: $P = \frac{V_{\max} I_{\max}}{2} \cos \theta$ 消耗的功率


imaginary 虚
 reactive power 无用功率 $Q = \frac{V_{\max} I_{\max}}{2} \sin \theta$ 来回流动的能量
 与相位差有关

power factor 功率因数 $PF = \cos(\theta_V - \theta_I)$



Complex power 复功率 $S = P + jQ \quad VA$

$$P = \operatorname{real}\{S\} \quad W = V I^*_{\# \text{ 有效}}, \quad \begin{bmatrix} |V| \angle \theta_V, |I| \angle \theta_I \\ |V| |I| \cos(\angle \theta_V - \theta_I) \\ e^{j(\theta_V - \theta_I)} \end{bmatrix}$$
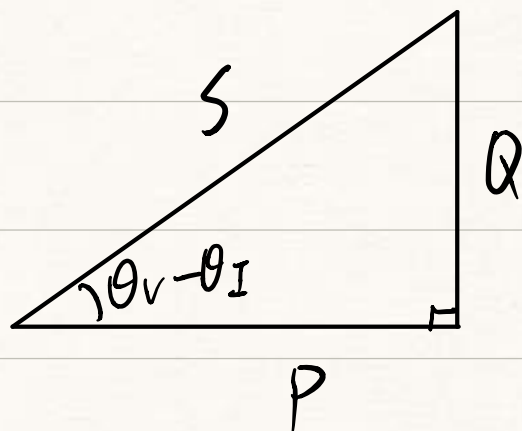
$$Q = \operatorname{img}\{S\} \quad VAR$$


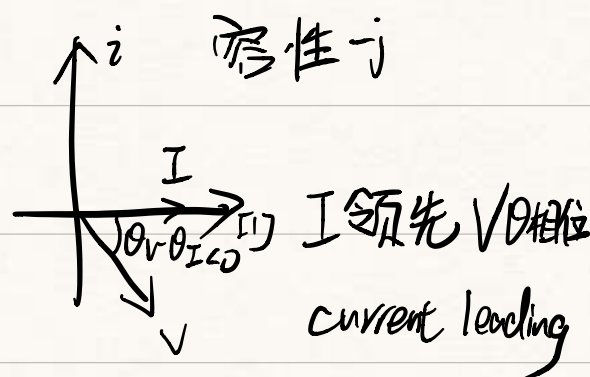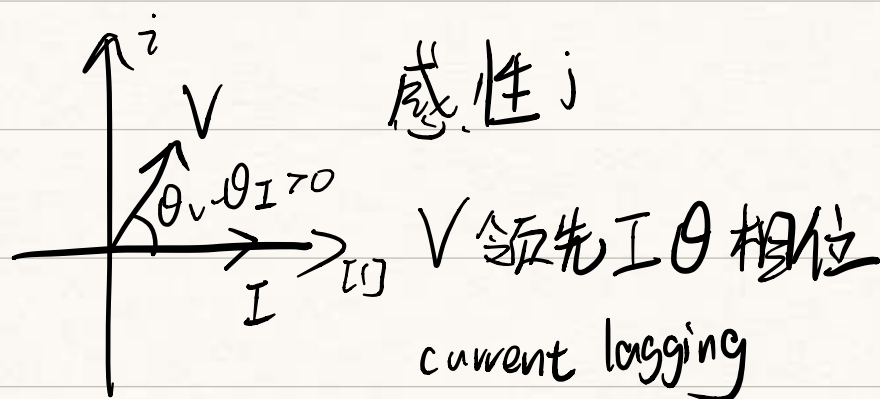
$$PF = \cos(\theta_V - \theta_I) = \frac{P}{S}$$



$$R \quad S_R = V I_R^* = \frac{V^2}{R}$$

$$L \quad S_L = V \cdot I_L^* = j \frac{V^2}{X_L}, j \frac{V^2}{\omega L}$$

$$C \quad S_C = V \cdot I_C^* = -j \frac{V^2}{X_C}, -j \omega C V^2$$

$$\text{Apparent Power 视在功率 } |S| = \sqrt{P^2 + Q^2} = |V||I|$$


Power factor correct or reactive compensation

功率因素校正

无功补偿

在电路中, PF 越近 1 越高效

nodal analysis 节点电流法 KCL 解复杂电路

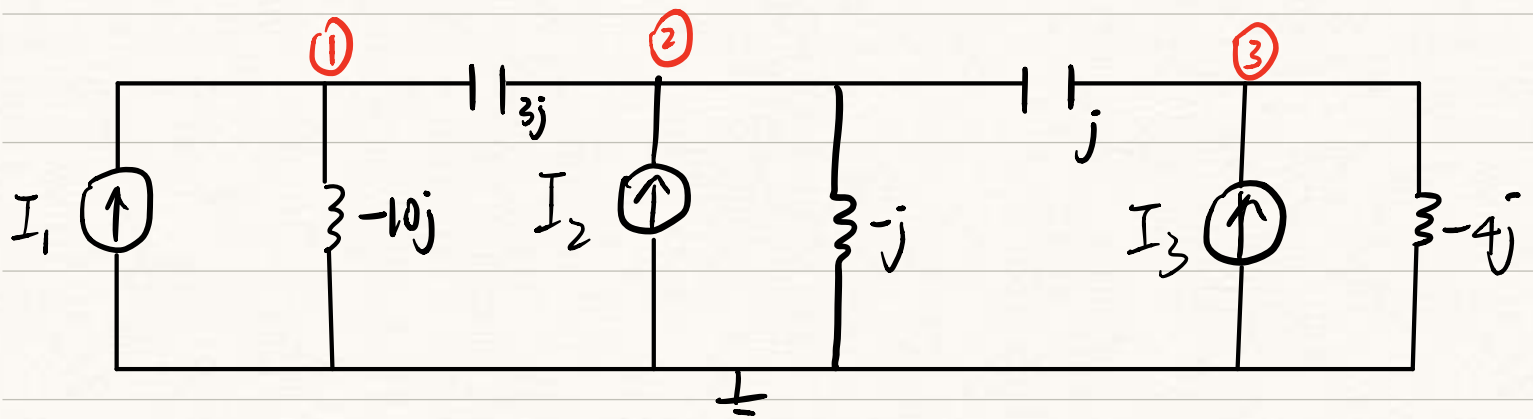

已知 admittances $Y = \frac{1}{Z}$ (S) 解方便计算

已知 $I_{1,2,3}$ 求 $V_{1,2,3}$

$$\textcircled{1}: (V_1 - V_2) \cdot 3j + (V_1 - 0)(-10j) - I_1 = 0$$

$$\textcircled{2}: (V_2 - V_1) \cdot 3j + (V_2 - 0)(-j) + (V_2 - V_3)j - I_2 = 0$$


$$\textcircled{3}: (V_3 - V_2) \cdot j + (V_3 - 0)(-4j) - I_3 = 0$$

$$\Rightarrow \begin{cases} I_1 = -7jV_1 - 3jV_2 \\ I_2 = -3jV_1 + 3jV_2 - 1jV_3 \\ I_3 = -1jV_2 - 3jV_3 \end{cases} \Rightarrow \begin{bmatrix} -7j & -3j & 0 \\ -3j & 3j & -j \\ 0 & -j & -3j \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix}$$

Y_{bus} : Bus admittance matrix V_{bus} I_{bus}

$$Y_{bus} \cdot V_{bus} = I_{bus}$$


Three phase system 三相电路

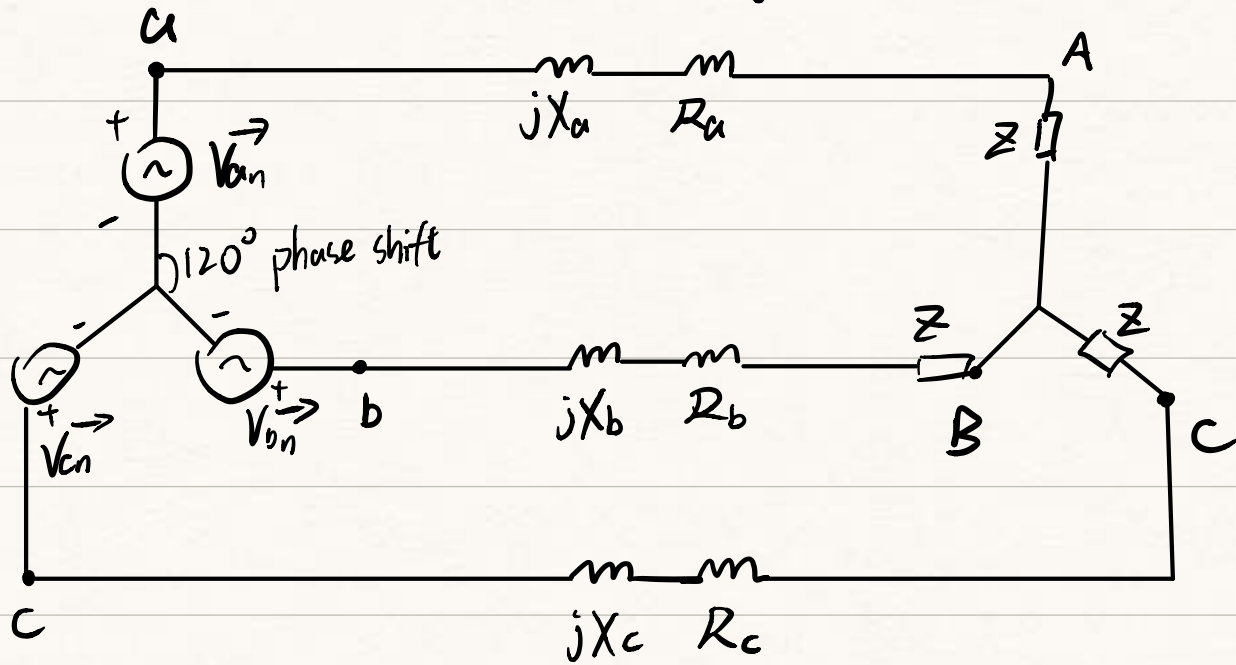

★ $\vec{V}_{an} = |V_{an}| \angle 0^\circ$, $\vec{V}_{bn} = |V_{bn}| \angle -120^\circ$, $\vec{V}_{cn} = |V_{cn}| \angle 120^\circ$, $R_a = R_b = R_c$

define $a = 1 \angle 120^\circ$ $V_{bn} = a^2 V_{an}$ $I_{bn} = a^2 I_{an}$
 $V_{cn} = a V_{an}$ $I_{cn} = a I_{an}$

Y型连接电路 wye (Y) connection

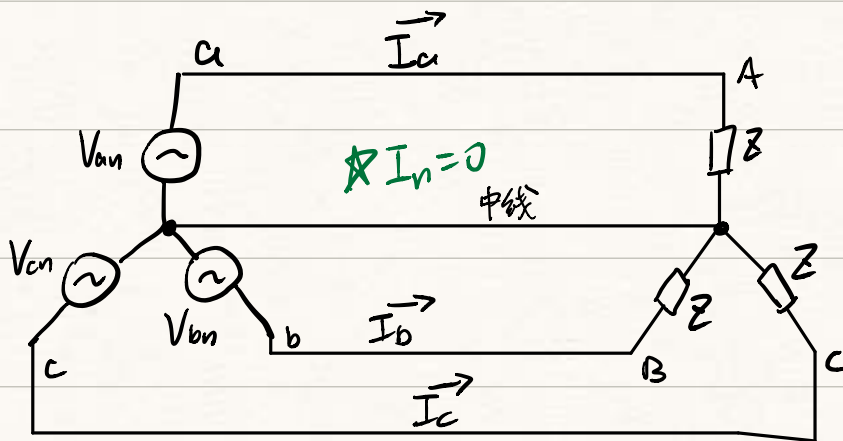

in balance system 平衡系统中
 no neutral current 无中性流,
 I总和为零

$$I_n = I_a + I_b + I_c = \frac{V}{Z} (\angle 0^\circ + \angle -120^\circ + \angle 120^\circ) = 0$$

$$S = V_{an} I_{an}^* + V_{bn} I_{bn}^* + V_{cn} I_{cn}^* = 3 V_{an} I_{an}^*$$

3 phase Complex Power $S_{3\phi} \equiv$ 三相功率

$$\begin{aligned} S_{3\phi} &= S_A + S_B + S_C = V_{an} I_a^* + V_{bn} I_b^* + V_{cn} I_c^* \\ &= V_{an} I_a^* + (\alpha^2 V_{an}) (\alpha^2 I_a)^* + (\alpha V_{an}) (\alpha I_a)^* \\ &= V_{an} I_a^* + \alpha^2 (\alpha^2)^* V_{an} I_a^* + \alpha \cdot \alpha^* V_{an} I_a \\ &= V_{an} I_a^* (1 + \underbrace{\alpha^2 \alpha^2}^1 + \underbrace{\alpha \alpha^*}^1) \\ &= 3 V_{an} I_a^* \end{aligned}$$

Phase Voltage: Voltage across each load (source) in each phase
三相(负载)电压 $\begin{cases} V_{an}, V_{bn}, V_{cn} \\ V_{AN}, V_{BN}, V_{CN} \end{cases}$ 三相负载上电压


phase current: current through load in each phase
三相(负载)电流 $\begin{cases} I_a, I_b, I_c \end{cases}$ 三相负载上电流

Line voltage (line to line Voltage): voltage difference between 2 phases
(传输间) 线电压 $\begin{cases} V_{ab} = V_{an} - V_{bn} \\ V_{bc} = V_{bn} - V_{cn} \\ V_{ac} = V_{an} - V_{cn} \end{cases}$ 传输线间相位电压差

Line current: currents through transmission line in each phase
(传输) 线电流 $\begin{cases} I_a, I_b, I_c \end{cases}$ 传输线上电流
Y 线电流 = 三相电流

Y线电压

Y connection - Line Voltage

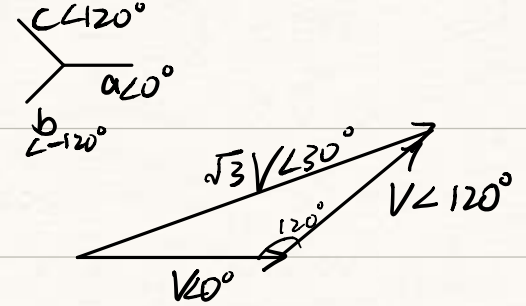


$$V_{ab} = V_{an} - V_{bn} = |V| (\angle 0^\circ - \angle -120^\circ) \\ = \sqrt{3} V_{an} \angle 30^\circ$$

$$V_{bc} = \sqrt{3} V_{bn} \angle 30^\circ = \sqrt{3} V_{an} \angle 30^\circ - 120^\circ = \sqrt{3} V_{an} \angle -90^\circ$$

$$V_{ca} = \sqrt{3} V_{cn} \angle 30^\circ = \sqrt{3} V_{an} \angle 30^\circ + 120^\circ = \sqrt{3} V_{an} \angle 150^\circ$$

三角型电路 Delta(Δ) connection

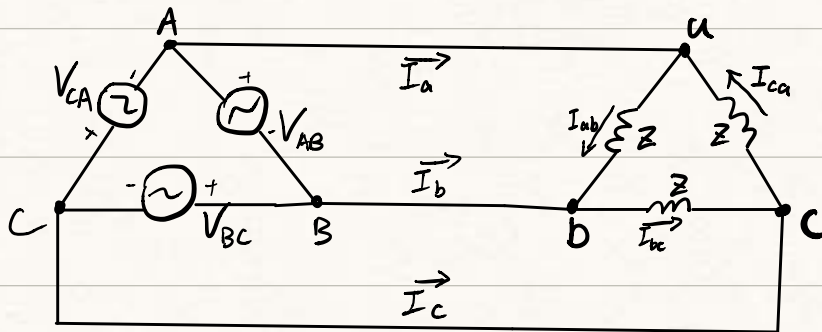

phase voltage 三相(线)电压

Δ 型三相电压=线电压

(V_{AB}, V_{BC}, V_{CA}) & (V_{ab}, V_{bc}, V_{ca})
电压 负载

line-line Voltage (传输) 线电压

(V_{AB}, V_{BC}, V_{CA}) & (V_{ab}, V_{bc}, V_{ca})
电压 负载

phase currents 三相(负载)电流

(I_{ab}, I_{bc}, I_{ca})


line currents (传输) 线电流

(I_a, I_b, I_c)

用KCL得 $I_a = I_{ab} - I_{ca}$

$$I_b = I_{bc} - I_{ab}$$

$$I_c = I_{ca} - I_{bc}$$

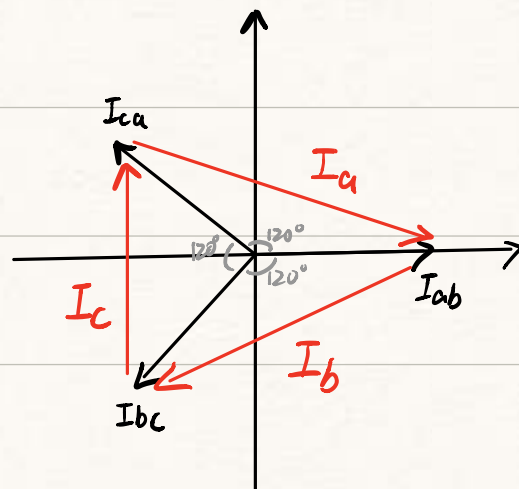

$$I_a = \sqrt{3} I_{ab} \angle -30^\circ$$


$$I_b = \sqrt{3} I_{bc} \angle -30^\circ$$

$$I_c = \sqrt{3} I_{ca} \angle -30^\circ$$

$$S_{3\phi} = 3 V_{\text{phase}} I_{\text{phase}}^*$$

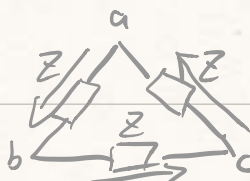例1) Δ -connected load with $Z = 120 \angle 30^\circ \Omega$ supplied by 3 ϕ 12kV (L-L) source. Find complex power in each phase of load
一定是有效值rms

$$V_{ab} = 12 \text{ kV} \angle 0^\circ \text{ set as ref}$$



$S_a = V_{ab} I_{ab}^*$ Δ 三相电压=线电压, 求负载功率用负载三相电流


$$I_{ab} = \frac{V_{ab}}{Z} = \frac{12 \text{ kV} \angle 0^\circ}{120 \angle 30^\circ} = 100 \angle -30^\circ \text{ (A)} \quad \begin{cases} I_{bc} = 100 \angle -30^\circ - 120^\circ = 100 \angle -150^\circ \\ I_{ca} = 100 \angle -30^\circ + 120^\circ = 100 \angle 90^\circ \end{cases}$$

$$S_a = V_{ab} \cdot I_{ab}^* = 1200 \text{ k} \angle 30^\circ$$


$$\text{和 } I_{a,b,c} \quad \begin{cases} I_a = \sqrt{3} I_{ab} \angle -30^\circ = 100\sqrt{3} \angle -60^\circ \text{ A} \\ I_b = \sqrt{3} I_{bc} \angle -30^\circ = 100\sqrt{3} \angle -180^\circ \text{ A} \\ I_c = \sqrt{3} I_{ca} \angle -30^\circ = 100\sqrt{3} \angle 60^\circ \text{ A} \end{cases}$$

Y-Δ Conversion 变化


分析 3 相系统时, 为简化, 只分析其中一条路线, 其余适用

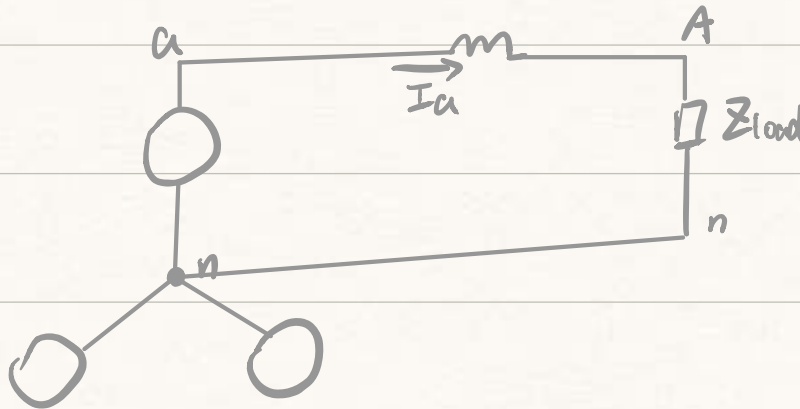
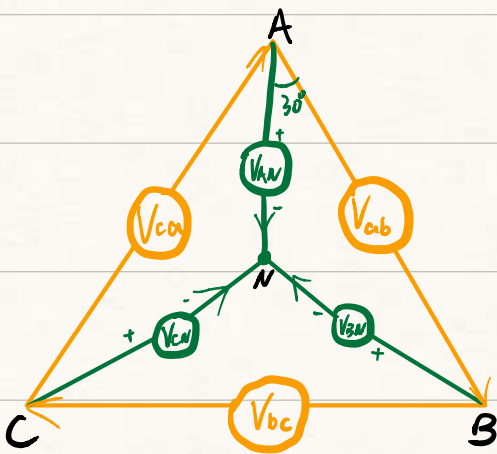
$$V_{AN} = \frac{V_{ab}}{\sqrt{3}} \angle -30^\circ$$



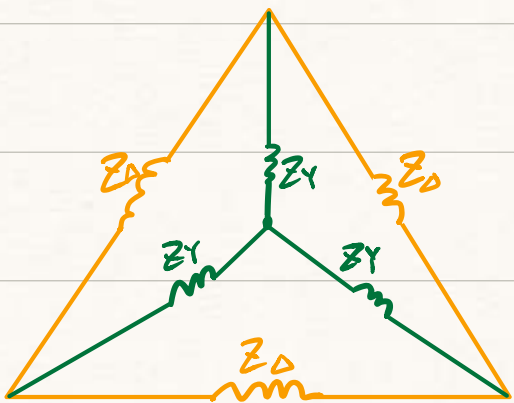
$$Z_Y = \frac{\frac{V_{phase}}{\sqrt{3}} \angle -30^\circ}{I_{phase} \sqrt{3} \angle -30^\circ} = \frac{Z_\Delta}{3}$$



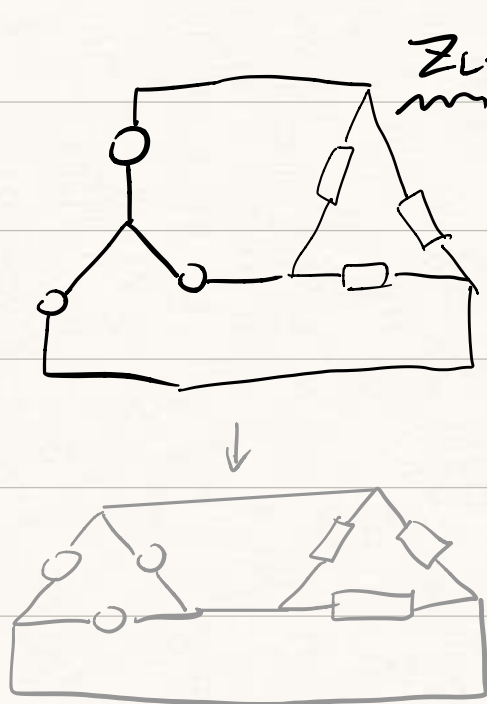
例 已知 Y 型电压 $V_{ab} = 480 \angle 0^\circ \text{ V}$

Δ 型负载 $Z_\Delta = 30 \angle 40^\circ \Omega$, line impedance 线路阻抗

为 $1 \angle 85^\circ \Omega$. 求线电流, Δ 负载电流, 电压


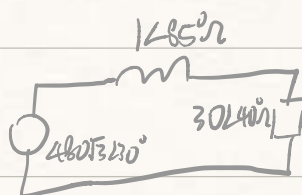
$$V_{ab}^\Delta = \sqrt{3} V_{ab} \angle 30^\circ$$
$$= 480\sqrt{3} \angle 30^\circ$$




$$I_a = \frac{V_{ab}^\Delta}{1 \angle 85^\circ + 30 \angle 40^\circ}$$

line (to line) Voltage phase Voltage

★所有给定三相问题电压都是两线差电压而不是到中线电压差

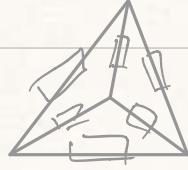
例 三相 线负载 $2+4j\Omega$ 源 60Hz , $120\sqrt{3}\text{V}$ 电压三相平衡了



1st Y型负载 $Z_{L1}^Y = 30+40j\Omega$

+ 2nd Δ 型负载 $Z_{L2}^\Delta = 60-45j\Omega$ $Z_{L2}^\Delta \xrightarrow{Y} Z_{L2}^Y = \frac{Z_{L2}^\Delta}{3} = 20-15j\Omega$

1) 求电流, 功率 real & reactive

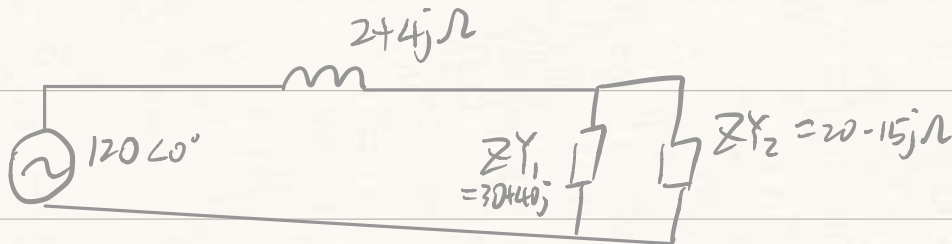

$$\text{assume } V_{AN} = \frac{120\sqrt{3}}{\sqrt{3}} \angle 0^\circ = 120 \angle 0^\circ \text{ V}$$

$$I_a = \frac{V_{AN}}{Z_{Y1} // Z_{Y2}} = \frac{120 \angle 0^\circ}{24} = 5 \angle 0^\circ \text{ A}$$

$$S_s = V_{AN} \times I_a^* = 120 \angle 0^\circ \cdot 5 \angle 0^\circ = 600 \text{ VA}, P_s = 600 \text{ W}, Q = 0$$

$$S_s^{3\phi} = 3S_s = 1800 \text{ VA} \quad P_s^{3\phi} = 3P_s = 1800 \text{ W}$$

three phase power instantaneous 三相功率瞬时值

$$v_{an}(t) = \sqrt{2} V_{LN} \cos(\omega t + \phi) \text{ V}$$

$$i_a(t) = \sqrt{2} I_L \cos(\omega t + \beta) \text{ A}$$

$$2 \cos a \cos b = \cos(a+b) + \cos(a-b)$$

$$P_a(t) = v_{an}(t) \cdot i_a(t) = 2 V_{LN} I_L \cos(\omega t + \phi) \cos(\omega t + \beta) \text{ W}$$


$$= V_{LN} I_L \cos(\phi - \beta) + V_{LN} I_L \cos(2\omega t + \phi + \beta) \text{ W}$$

$$P_{3\phi}(t) = P_a(t) + P_b(t) + P_c(t)$$

$$= 3 V_{LN} I_L \cos(\phi - \beta) + V_{LN} I_L \left[\begin{aligned} &\cos(2\omega t + \phi + \beta) \\ &+ \cos(2\omega t + \phi + \beta - 240^\circ) \\ &+ \cos(2\omega t + \phi + \beta + 240^\circ) \end{aligned} \right]$$

^{LN}
line to neutral $P_{3\phi}(t) = \underline{3 V_{LN} I_L \cos(\phi - \beta) \text{ W}}$ 三相电压

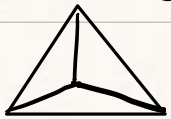^{LL}
Line to line $P_{3\phi}(t) = \underline{\sqrt{3} V_{LL} I_L \cos(\phi - \beta) \text{ W}}$ 线电压



三相电压瞬时值为常数

磁场 H、B 计算


安培定律 Ampere's Law

$$\oint H dl = \sum I_{enc}$$

例:

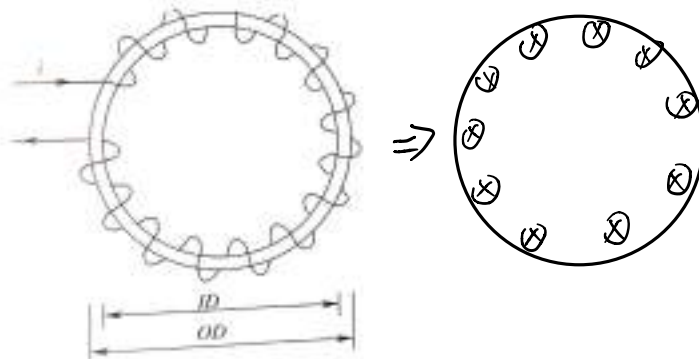Example:

Consider a coil which has $N=25$ turns and the toroid has an inside diameter of $I_D=5\text{cm}$ and outside diameter of $O_D=5.5\text{cm}$. For a current $i=3\text{A}$, calculate the field intensity H along the mean-path length within the toroid.



$$d = \frac{I_D + O_D}{2} = 5.25\text{cm}, \quad \oint H dl = NI,$$

$$2\pi r_m = 0.165\text{m}$$

$$H = \frac{NI}{2\pi r_m} = \frac{25 \times 3}{0.165\text{m}} = 454.5\text{ A/m}$$

磁感应强度 $B = \mu_0 H$ ($\mu_0 = 4\pi \times 10^{-7} \text{ H/m}$)

(又叫磁通量密度) B : flux density 单位 Tesla 特斯拉

磁通量 $\Phi = \int_S B \cdot d\mathbf{s} = BA$ (垂直面积)

Φ : flux 单位 Wb 韦伯

ferromagnetism 强磁性, μ 仅在小区间呈线性

磁通势 Magnetomotive force $\text{mmf} = Hl = \Phi \cdot R = NI$


$$\begin{cases} B = \mu H \\ \Phi = B \cdot A \end{cases} \Rightarrow \text{mmf} = \Phi \cdot \boxed{\frac{l}{\mu A}}$$

定义 reluctance 磁阻 $R = \frac{l}{\mu A}$

例:

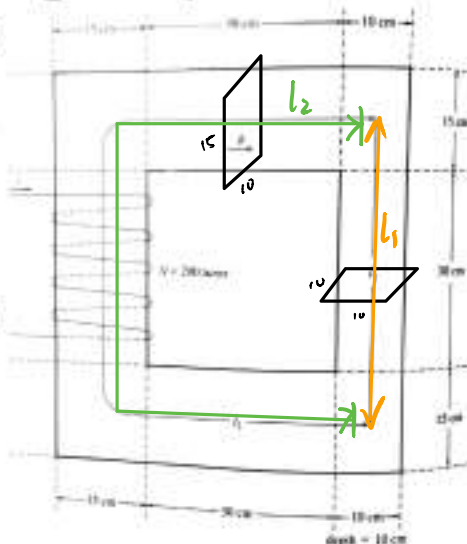Example 1 (class assignment)

A ferromagnetic core has three sides of uniform width and a thinner side. The depth of the core (into the page) is 10 cm, and other diameters are as shown. This is a 200-turn coil wrapped around the left side of the core. Assuming $\mu_r = 2500$, how much flux will be produced by 1 (A) current?



$$l_1 = 30 + \frac{15}{2} + \frac{15}{2} = 45 \text{ cm}$$

$$R_1 = \frac{l_1}{\mu A_1} = \frac{60 \times 10^{-2} \text{ m}}{2500 \times 4\pi \times 10^{-7} \times 0.1^2 \text{ m}^2} = 14323.9$$

$$l_2 = 30 + \frac{15}{2} + 30 + \frac{15}{2} + \frac{15}{2} + 30 + \frac{15}{2} + \frac{10}{2} + \frac{10}{2} = 130 \text{ cm}$$

$$A_2 = 15 \times 10 = 0.015 \text{ m}^2$$


$$R_2 = \frac{l_2}{\mu A_2} = \frac{130 \times 10^{-2} \text{ m}}{2500 \times 4\pi \times 10^{-7} \times 0.015 \text{ m}^2} = 27586.9$$

reluctance are in serial

$$\Phi = \frac{NI}{R_{\text{total}}} = \frac{200 \times 1 \text{ A}}{R_1 + R_2} = 0.0048 \text{ wb}$$

flux linkage 磁链 $\lambda = N \cdot \Phi = Li$
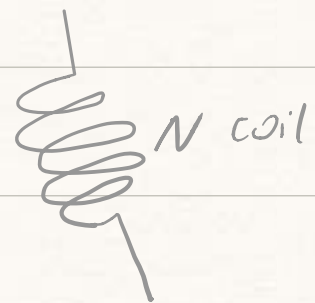
$$\begin{cases} L = \frac{\lambda}{i} \\ \lambda = N\Phi \\ \Phi = \frac{Ni}{R} \end{cases} \Rightarrow L = \frac{N^2}{R}$$



Faraday's Law 法拉第电磁感应定律


变化磁通量产生电压

$$V = \frac{d\lambda}{dt} = \frac{dN\Phi}{dt}$$

Lenz's Law 楞次定律

感应电流的磁场总要阻碍磁场变化

leakage flux
磁泄露

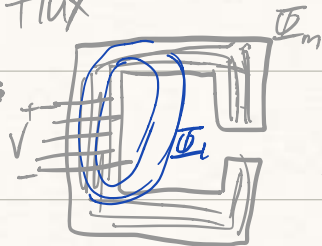

$$\Phi = \Phi_m + \Phi_l$$


↑ ↑
magnet flux leakage flux

$$\lambda = N\Phi = \lambda_m + \lambda_l$$

$$L = \frac{\lambda}{i} = L_m + L_l$$

↑ ↑
magnet inductance leakage inductance

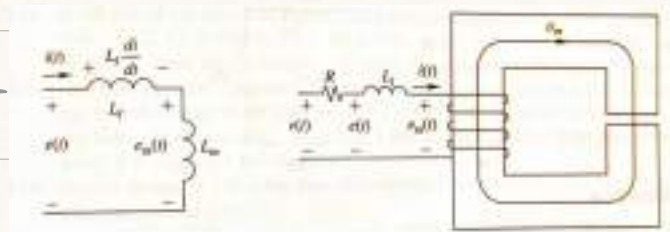
计入磁泄露, $V = L_m \frac{di}{dt} + L_l \frac{di}{dt}$



理想变压器 ideal transformer



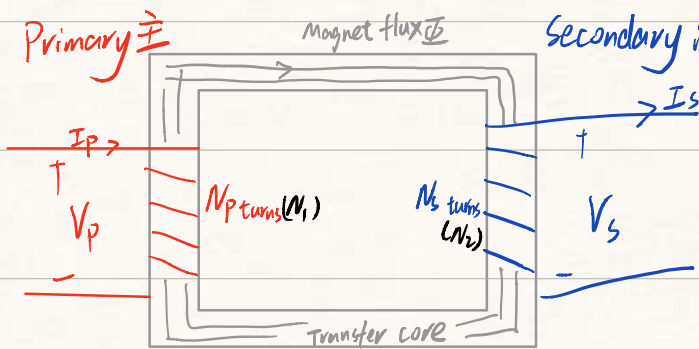线圈比
turn ratio $a_t = \frac{N_p}{N_s} = \frac{N_1}{N_2}$



理想变压器

1. 无功率损耗 no power loss $P_{in} = P_{out}$
2. 磁芯 μ 无限大 permeability infinite $\mu \rightarrow \infty R \rightarrow 0$
3. 无磁泄露 no leakage flux

简写




$$N_1 I_1 = N_2 I_2 = Hl$$

$$\frac{V_1}{N_1} = \frac{V_2}{N_2}$$

Secondary impedance referred to primary side:

副线圈在主电路的等效电阻

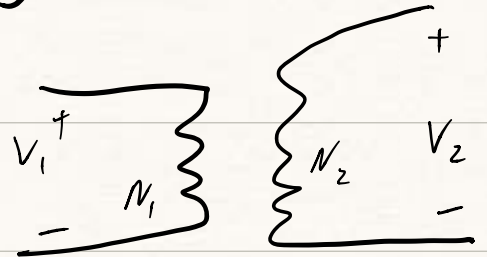known $\begin{cases} \frac{V_1}{V_2} = \frac{N_1}{N_2} \\ \frac{I_1}{I_2} = \frac{N_2}{N_1} \end{cases}, P_1 = P_2$



$$Z_{2ref} = \frac{V_1}{I_1} = \frac{a V_2}{\frac{1}{a} I_2} = a^2 Z_2 = \left(\frac{N_1}{N_2}\right)^2 Z_2$$

Example 3

- Calculate the impedance of the load on the secondary of an ideal transformer and its value referred to the primary side.

$N_1=2000$; $N_2=500$; $V_1=1200\angle 0^\circ(\text{V})$; $I_1=5\angle -30^\circ(\text{A})$;

$$\left\{ \begin{array}{l} \frac{V_1}{V_2} = \frac{N_1}{N_2} \\ \frac{I_1}{I_2} = \frac{N_2}{N_1} \end{array} \right. , \text{ so } \quad V_2 = \frac{N_2}{N_1} \cdot V_1 = 300\angle 0^\circ \text{ V}$$
$$I_2 = \frac{N_1}{N_2} \cdot I_1 = 20\angle -30^\circ (\text{A})$$

$$Z_2 = \frac{V_2}{I_2} = 15\angle 30^\circ (\Omega)$$

$$Z_2' = Z_2 \cdot \left(\frac{N_1}{N_2}\right)^2 = 16 Z_2$$
$$= 240\angle 30^\circ (\Omega)$$

Practical transformer 实际变压器

计算实际磁损失 ($\Phi = \frac{NI}{R_{\text{total}}}$, E_1, E_2 线圈电压)

$$\begin{cases} N_1 I_1 - N_2 I_2 = R_c \Phi_c \\ \Phi_c = \frac{E_1}{j\omega N_1} \end{cases}$$


$$\Rightarrow N_1 I_1 - N_2 I_2 = \frac{E_1 R_c}{j\omega N_1}$$

$$I_1 = \frac{N_2}{N_1} \cdot I_2 + \frac{R_c}{N_1} \left(\frac{E_1}{j\omega N_1} \right)$$

$$I_m = \frac{R_c E_1}{j\omega N_1^2} \quad \text{magnetizing current} \\ \text{磁化电流}$$

$$= \frac{N_2}{N_1} \cdot I_2 - j \left(\frac{R_c}{j\omega N_1^2} \right) E_1$$

B_m 似电感、阻抗、导纳

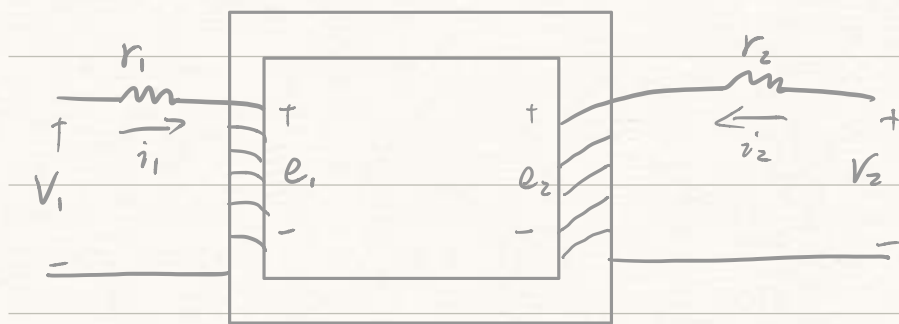

自感.互感.

$$V_1 = i_1 r_1 + e_1, \quad V_2 = i_2 r_2 + e_2$$

假设 i_1 acting alone

假设 i_2 acting alone

flux linkage $\lambda_{11} = N_1 \Phi_{11} = L_{11} i_1$

$$\lambda_{22} = N_2 \Phi_{22} = L_{22} i_2$$

$$\lambda_{21} = N_2 \Phi_{21} = L_{21} i_1$$

$$\lambda_{12} = N_1 \Phi_{12} = L_{12} i_2$$

Self Inductance

Mutual Inductance

自感系数

互感系数 $L_{12} = L_{21}$

$$\Rightarrow \begin{cases} \lambda_1 = \lambda_{11} + \lambda_{12} \\ \lambda_2 = \lambda_{22} + \lambda_{21} \end{cases} \Rightarrow \begin{cases} \lambda_1 = L_{11} i_1 + L_{12} i_2 \\ \lambda_2 = L_{22} i_2 + L_{21} i_1 \end{cases}$$


时域

$$\begin{cases} V_1 = i_1 r_1 + L_{11} \frac{di_1}{dt} + L_{12} \frac{di_2}{dt} \\ V_2 = i_2 r_2 + L_{22} \frac{di_2}{dt} + L_{21} \frac{di_1}{dt} \end{cases}$$


频域

$$\begin{cases} V_1 = \underbrace{(r_1 + j\omega L_{11})}_{Z_{11}} \cdot i_1 + \underbrace{j\omega L_{12}}_{Z_{12}} \cdot i_2 \\ V_2 = \underbrace{(r_2 + j\omega L_{22})}_{Z_{22}} \cdot i_2 + \underbrace{j\omega L_{21}}_{Z_{21}} \cdot i_1 \end{cases}$$

等价 equivalent circuit

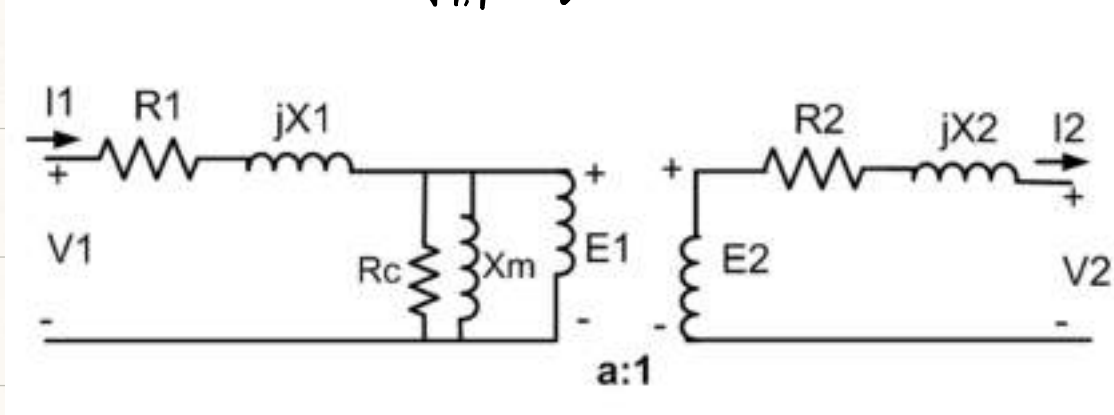

简化变压器

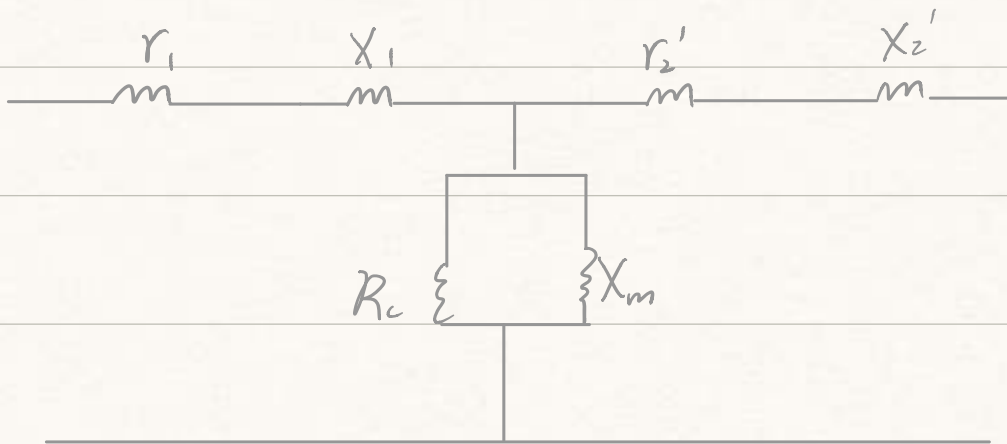

$$(a = \frac{N_1}{N_2})$$

referred to the primary side

$$r_2' = a^2 r_2 \quad r_e = r_1 + r_2'$$

$$X_2' = a^2 X_2 \quad X_e = X_1 + X_2'$$


计算参数 parameters

① 开路 open circuit test

X_m 磁感应阻抗 magnet resistance

R_c 磁泄露 core losses

副线圈断路求 I_1 和 P_{loss}

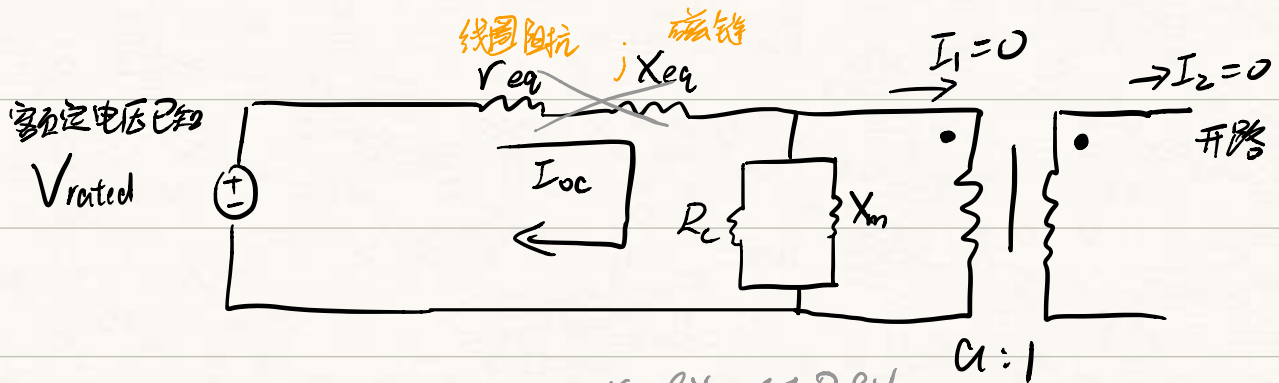

$$P_{loss} = \frac{V_c^2}{R_c} \quad (R_c = \frac{1}{G_c})$$


$r_{eq} \& X_{eq} \ll R_c \& X_m$

$$V_2 = V_{rated}$$

$$I_{oc} = \frac{V_{rated}}{R_c + jX_m}$$

② 短路 short circuit test

副线圈短路测 V_{rated} 和 P_{loss}

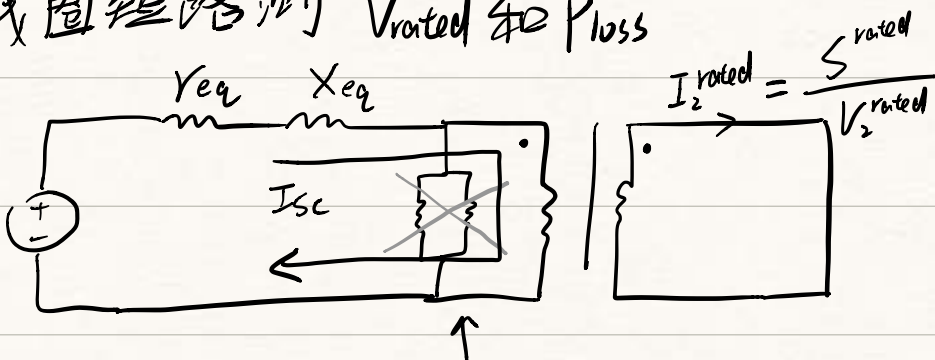

输入电压很小, 所以电流在磁化分支很小, 忽略不计
magnetizing branch

$$P_{loss} = r_{eq} \cdot I_{sc}^2$$

$$Z_{eq} = r_{eq} + jX_{eq} = \frac{V_{sc}}{I_{sc}} \text{ 可求 } V_{sc}$$

Example: Model Parameter Calculation

A single phase, (100 MVA, 200/80 kV) transformer has the following test data:

open circuit: 20 amps, with 10 kW losses

short circuit: 30 kV, with 500 kW losses

Find the model parameters.

例 open circuit test

$$V_{oc} = V_1^{rated} = 200 \text{ kV}$$

$$P_{loss} = \frac{V_{oc}^2}{R_c} = G_c \cdot V_{oc}^2$$

$$\Rightarrow G_c = 25 \times 10^{-8}, R_c = 4 \text{ M}\Omega$$

Short circuit

$$I_{sc} = I_1^{rated} = \frac{S_{rated}}{V_1^{rated}} = \frac{100 \text{ MVA}}{200 \text{ kV}} = 500 \text{ A}$$

$$r_{eq} = \frac{P_{loss}}{I_{sc}^2} = \frac{500 \text{ kW}}{500^2} = 2 \Omega$$

$$|Z_{eq}| = \frac{V_{sc}}{I_{sc}} = \frac{30 \text{ kV}}{500 \text{ A}} = 60 \Omega$$

$$X_{eq} = \sqrt{Z_{eq}^2 - r_{eq}^2} = 59.96 \Omega$$

rated 额定电压, 以实际值为准

Per unit system (pu.) 标么值

actual quantity 实际值

$$\text{quantity per unit 标么值} = \frac{\text{base value of quantity 基准值}}{\text{base value of quantity 基准值}} \quad [\text{pu.}]$$
$$S_{pu} = \frac{S}{S_b}$$

怎么选基准值 Base value? (base 缩写 b 标, S_b, V_b)


先选 S_b, V_b

$$I_b = \frac{S_b}{V_b}, \quad Z_b = \frac{V_b}{I_b} = \frac{V_b^2}{S_b^2}$$

X 值 $X = 2\% = \frac{X_{\text{actual}}}{Z_{\text{base}}}$, $Z_{\text{base}} = \frac{V_{\text{rated}}^2}{S_{\text{rated}}}$ 假设 $S_b = S_{\text{rated}}, V_b = V_{\text{rated}}$

变压器标么值按线圈比例关联 $\frac{V_{b1}}{V_{b2}} = \frac{N_1}{N_2} = a_t$, (S_b 相同)

主副端可选

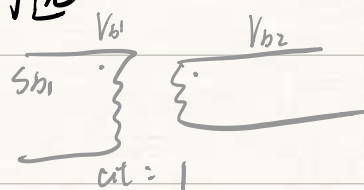

$$Z_{b1} = \frac{V_{b1}^2}{S_b}, \quad I_{b1} = \frac{S_b}{V_{b1}}$$

$$Z_{b2} = \frac{V_{b2}^2}{S_b} = \frac{1}{a_t^2} Z_{b1}, \quad I_{b2} = \frac{S_b}{V_{b2}} = a_t I_{b1}$$

bLV 即 phase Low Voltage bHV 即 phase High Voltage

$$Z_{bLV} = \frac{V_{bLV}}{I_{bLV}} = \frac{V_{bLV}^2}{S_b}$$

$$Z_{bHV} = \frac{V_{bHV}}{I_{bHV}} = \frac{V_{bHV}^2}{S_b}$$

S_b 复功率保持不变


$$\begin{cases} S_{pu} = \frac{S}{S_b} = V_{pu} I_{pu}^* \\ P_{pu} = \frac{P}{S_b} = V_{pu} I_{pu} \cos \theta \\ Q_{pu} = \frac{Q}{S_b} = V_{pu} I_{pu} \sin \theta \end{cases}$$

例:

$$Z\% = Z_{pu} \times 100\%$$

leakage of transformer is 10%, given $X = 10\% = 0.1 (pu.)$

$$R_{eq} = 2\% = 0.02 (pu.)$$

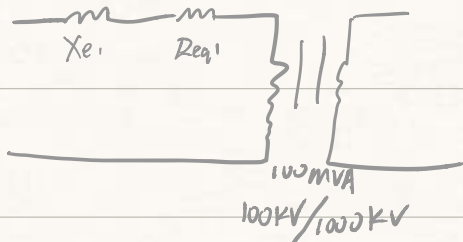

$$\text{则 } S_b = S_{rated} = 100 \text{ MVA}$$

$$V_{b1} = 100 \text{ KV}$$

$$\text{得 } Z_{b1} = \frac{V_{b1}^2}{S_b} = 100 \Omega$$

$$R_{eq1} = Z_{b1} \cdot R_{eq}(pu.) = 2 \Omega$$

$$X_{e1} = Z_{b1} \cdot X(pu.) = 10 \Omega$$

例: $V_{rated} = 120 \text{ V}, S_{rated} = 500 \text{ VA}$

If V applied across the load twice the rated v_{he}
and load draws rated power. 算 I

1) choose base value

$$V_b = 120 \text{ V}$$

$$S_b = 500 \text{ VA}$$

$$I_b = \frac{S_b}{V_b} = \frac{500}{120} = 4.167 \text{ A}$$

2) convert to pu.

$$V_{load} = \frac{240}{120} = 2(\text{pu.}), I_{load} = \frac{500}{V_{load}} = 0.5(\text{pu.})$$

$$P_{load} = \frac{P}{S_b} = V_{pu} I_{pu} \cos \theta = 1 \text{ pu.}$$

如果原 S_b, V_b 不一致, 反过来按比例算 Z_{pu}

$$\frac{Z_{pu2}}{Z_{pu1}} = \frac{\frac{Z_{actual}}{Z_{b2}}}{\frac{Z_{actual}}{Z_{b1}}} = \frac{Z_{b1}}{Z_{b2}}$$

'old' 'new'

$$\Rightarrow Z_{pu2} = \frac{Z_{b1}}{Z_{b2}} \cdot Z_{pu1}$$

★ 不同 base 转换 (考)

1 old
2 new

$$V_{pu} = \frac{V_{actual}}{V_{base}} \text{ 与 } V_{base} \text{ 反比}$$

$$PQS_{pu} = \frac{PQS}{S_{base}} \text{ 与 } S_{base} \text{ 反比}$$

$$ZXR_{pu} = \frac{V_{base}^2}{S_{base}} \text{ 与 } \frac{V_{base}^2}{S_{base}} \text{ 成正比}$$

$$(P, Q, S)_{pu \text{ on base 2}} = (P, Q, S)_{pu \text{ on base 1}} \cdot \frac{S_{base1}}{S_{base2}}$$

$$V_{pu \text{ on base 2}} = V_{pu \text{ on base 1}} \cdot \frac{V_{base1}}{V_{base2}}$$

$$(R, X, Z)_{pu \text{ on base 2}} = (R, X, Z)_{pu \text{ on base 1}} \cdot \frac{V_{base1}^2}{V_{base2}^2} \cdot \frac{1}{\frac{S_{base1}}{S_{base2}}}$$

$\frac{V^2}{S}$

例:

$$X_{L1} (\text{old}) = 0.02 (\text{p.u.}) \quad X_{L1} (\text{new}) = ?$$


$$R_1 (\text{old}) = 0.05 (\text{p.u.}) \quad R_1 (\text{new}) = ?$$

$$V_{1\text{base}} = 500 \text{ V} \quad S_{1\text{base}} = 100 \text{ MVA}$$

$$V_{2\text{base}} = 400 \text{ V} \quad S_{2\text{base}} = 50 \text{ MVA}$$

$$X_{L1}^{\text{new}} (\text{p.u.}) = 0.02 \times \frac{V_{1\text{base}}^2}{V_{2\text{base}}^2} \times \frac{S_{2\text{base}}}{S_{1\text{base}}} = 0.02 \times \frac{500^2}{400^2} \times \frac{50}{100} = 0.156 (\text{p.u.})$$


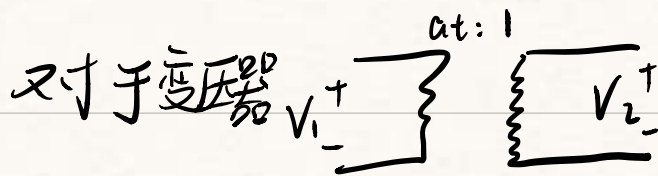
$$R_1^{\text{new}} (\text{p.u.}) = 0.05 \times \left(\frac{500}{400}\right)^2 \times \frac{50}{100} = 0.391 (\text{p.u.})$$



$$\text{实际} \frac{V_1}{V_2} = \frac{V_{1\text{p.u.}}}{V_{2\text{p.u.}}} = \frac{V_{1\text{base}}}{V_{2\text{base}}} = a_t$$

且有任何情况下副线圈 $Z_{\text{p.u.1}} = Z_{\text{p.u.2}}$

不受 Leakage 和电阻影响

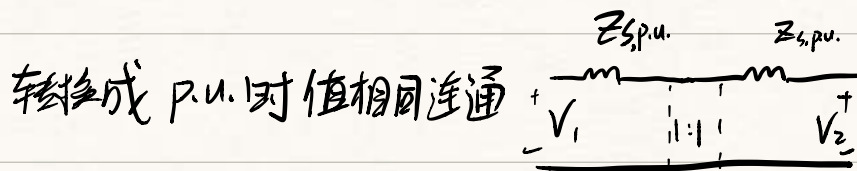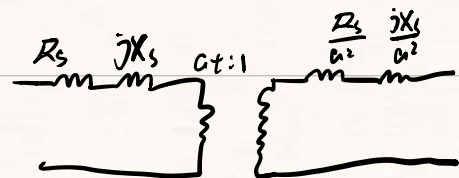


base 值代表一整片区域的基准值, 只会随变压器比例变化

同区域所有元件 base 值一致, $V_{\text{base}}^{\text{gen}}$, $V_{\text{base}}^{\text{trans}}$, $V_{\text{base}}^{\text{dis}}$ 用于所有计算

Transmission Line


Short: 小于 30km

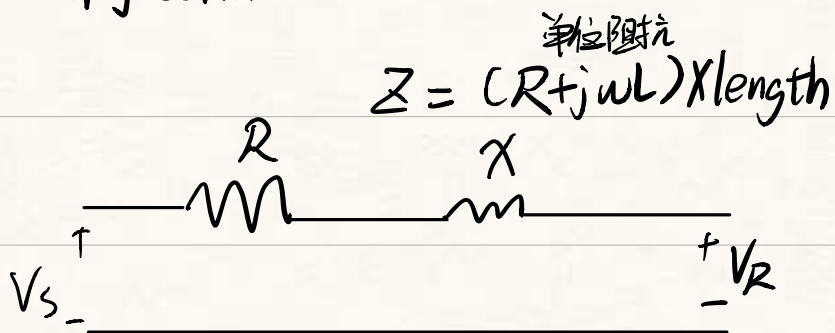

$$\begin{bmatrix} V_s \\ I_s \end{bmatrix} = \begin{bmatrix} 1 & Z \\ 0 & 1 \end{bmatrix} \begin{bmatrix} V_R \\ I_R \end{bmatrix}$$


Y_{bus}

Medium length: 大于 80km 小于 250km

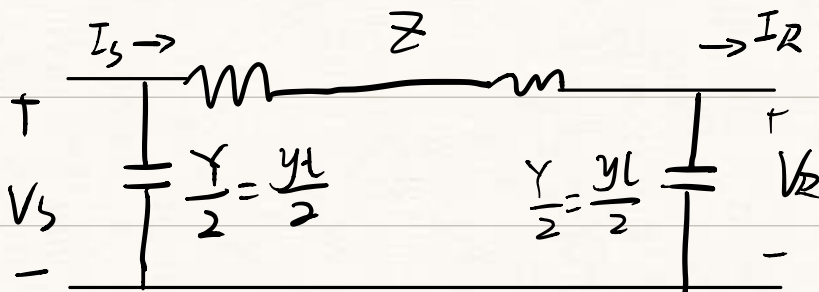

$$\begin{bmatrix} V_s \\ I_s \end{bmatrix} = \begin{bmatrix} (1 + \frac{YZ}{2}) & Z \\ Y(1 + \frac{YZ}{4}) & (1 + \frac{YZ}{2}) \end{bmatrix} \begin{bmatrix} V_R \\ I_R \end{bmatrix}$$

Long Length: $\neq 250\text{km}$

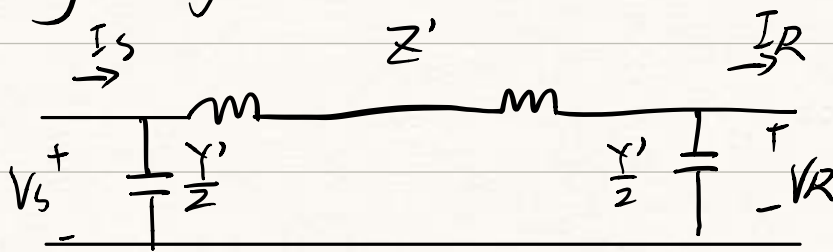

$$\frac{Y'}{2} = \frac{Y}{2} \left[\frac{\tanh \frac{\gamma l}{2}}{\frac{\gamma l}{2}} \right] S$$

$\gamma = \sqrt{ZY}$ Propagation Constant

$$Z' = Z \left[\frac{\sinh(\gamma l)}{\gamma l} \right] \Omega$$

$Z_c = \sqrt{\frac{Z}{Y}}$ Impedance