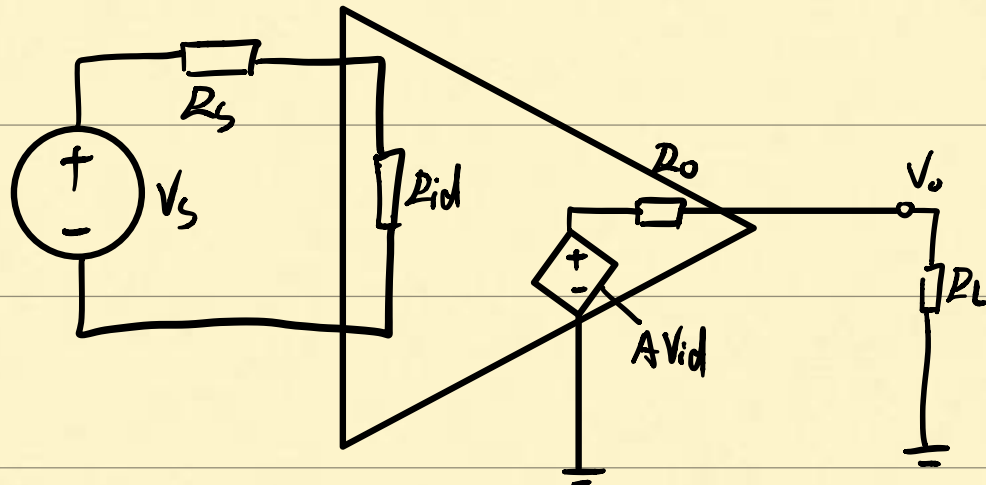


Q₁: A differential amplifier, connected in the circuit.

$$A = 84 \text{ dB}, R_{id} = 2 \text{ M}\Omega, R_o = 50 \Omega$$

$$\text{Sinusoidal signal } V_s(t) = V_s \cdot \sin(\omega_s t), R_s = 10 \text{ k}\Omega, R_L = 500 \Omega$$



a) Find the overall voltage A_v , current A_i , and power gain A_p for the amplifier and express it in dB.

	A_v	A_i	A_p
Gain ratio	14336.5	5.73×10^7	8.26×10^{11}
Gain [dB]	83.13	155.2	119.17

$$A_v = \frac{V_o}{V_s} = \frac{A_{Vid} \cdot \frac{R_L}{R_o + R_L}}{V_s} = \frac{A \cdot V_s \cdot \frac{R_{id}}{R_s + R_{id}} \cdot \frac{R_L}{R_o + R_L}}{V_s} = A \cdot \frac{R_{id}}{R_s + R_{id}} \cdot \frac{R_L}{R_o + R_L}$$

$$= 10^{\left(\frac{84}{20}\right)} \cdot \frac{2 \text{ M}}{10 \text{ k} + 2 \text{ M}} \cdot \frac{500}{50 + 500} = 14336.5$$

$$A_{v\text{-dB}} = 20 \lg |A_v| = 83.13$$

$$A_i = \frac{I_{out}}{I_{in}} = \frac{\frac{V_o}{R_L}}{\frac{V_s}{R_s + R_{id}}} = \frac{V_o}{V_s} \cdot \frac{R_s + R_{id}}{R_L} = 14336.5 \cdot \frac{10K + 2m}{500} = 5.73 \times 10^7$$

$$A_{i-dB} = 20 \lg |A_i| = 155.2$$

$$A_p = A_i \cdot A_v = 8.26 \times 10^{11}$$

$$A_{p-dB} = 10 \lg A_p = 119.17$$

b) 已知 peak to peak is 10V in $V_o(t)$

$$A = 5V$$

	$V_s(t)$	$A_v = V_o/V_s$	$V_o(t)$
differential amp	$0.348 \sin(\omega t) mV$	14336.5	$5 \sin(\omega t) V$

c) power, peak to peak is 10V in $V_o(t)$

	input power	output power	dissipated power
differential amp	$3.01 \times 10^{-14} W$	$0.0025 W$	$2.5 mW$

★RMS有效值

$$P_s = \frac{\left(\frac{V_s}{\sqrt{2}}\right)^2}{R_s + R_{id}} = 3.01 \times 10^{-14} W$$

$$P_o = \frac{\left(\frac{V_o}{\sqrt{2}}\right)^2}{R_L} = 0.0025 W = 2.5 mW$$


$$P_{dissipated} = P_{R_{id}} + P_{R_o}$$

$$= \frac{\left(\frac{V_s}{\sqrt{2}}\right)^2}{R_{id}} + \left(\frac{V_o}{A}\right)^2 \cdot R_o$$

$$= 3.0276 \times 10^{-14} + 0.0025$$

$$\approx 2.5 mW$$

Q2: Consider the amp circuit

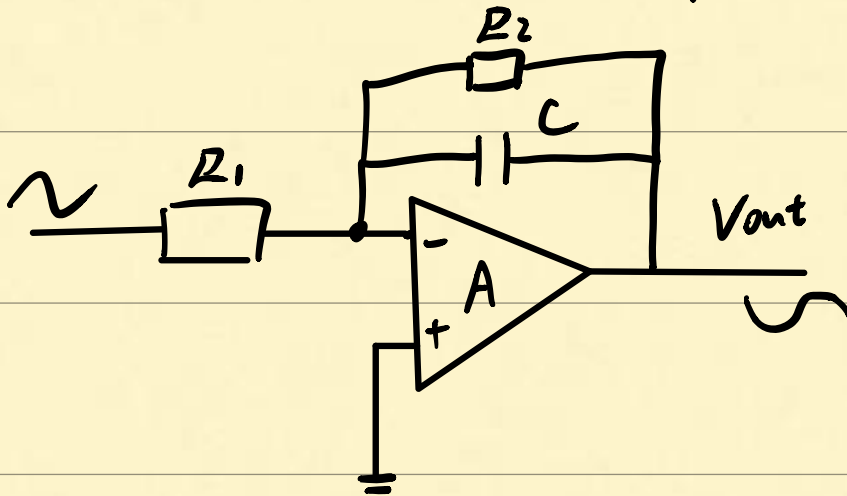

a) what is the transfer function $A_v(s) = V_o(s)/V_i(s)$?
 what is the circuit bandwidth frequency ω_B ? and
 unity gain frequency ω_T ?

$$A_v = \frac{V_{out}}{V_{in}} = -\frac{R_2 // \frac{1}{sC}}{R_1} = -\frac{R_2}{R_1} \cdot \frac{1}{1 + sCR_2}$$

$$\omega_B = \frac{1}{R_2 C}$$

让 A_v 为 $\frac{1}{\sqrt{2}}$ 倍 则 $\begin{matrix} s=j\omega_B \\ sCR_2=1 \end{matrix} \Rightarrow \omega_B = \frac{1}{R_2 C}$

$$\omega_T = \underline{A_v(0)} \cdot \omega_B = -\frac{1}{R_1 C}$$

★


when $R_1 = 3.3k\Omega$, $R_2 = 390k\Omega$, $C = 10pF = \dots$

so $A_v(0) = 118.18$, $A_{v-dB} = 20\lg|A_v(0)| = 41.45$

$\omega_B = 256.41 \text{ K rad/s} \Rightarrow f_B = 40.81 \text{ KHz}$

$\omega_T = 3.03 \times 10^7 \text{ rad/s} \Rightarrow f_T = 4.822 \text{ MHz}$

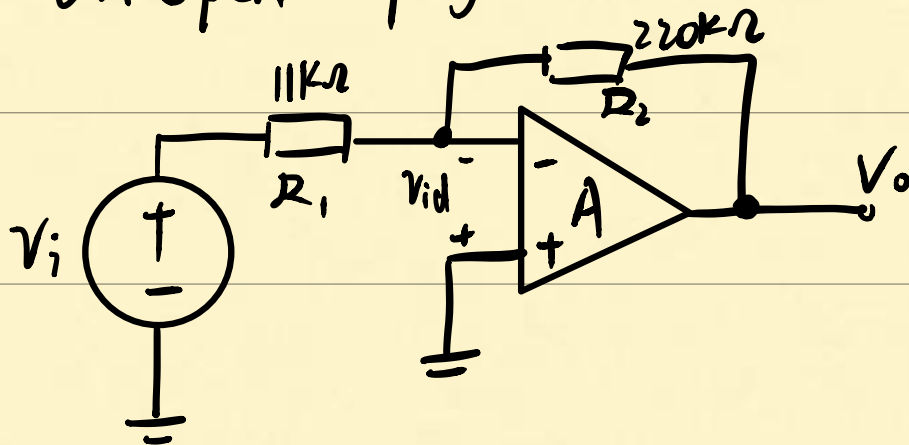Q3: An inverting amp is built using an op-amp with an open loop gain of 60dB.



a) What are the ideal closed loop gain, loop gain, and actual closed loop gain for this amp if $R_1 = 11k\Omega$ $R_2 = 220k\Omega$.
 $A = 10^{\left(\frac{60}{20}\right)} = 1000$

ideal closed loop gain $A_v^{ideal} = -\frac{R_2}{R_1} = -20$

feedback $\beta = \frac{R_1}{R_1 + R_2} = 0.04762$


loop gain $T = A \cdot \beta = 47.619$

actual closed loop gain $A_v^{actual} = A_v^{ideal} \cdot \frac{T}{1+T}$
 $(A_v) = -19.589$

when $R_1 = 3.3k\Omega$, $R_2 = 390k\Omega$

$A_v^{ideal} = -118.182$, $T = A \cdot \beta = 8.391$, $A_v = -105.597$

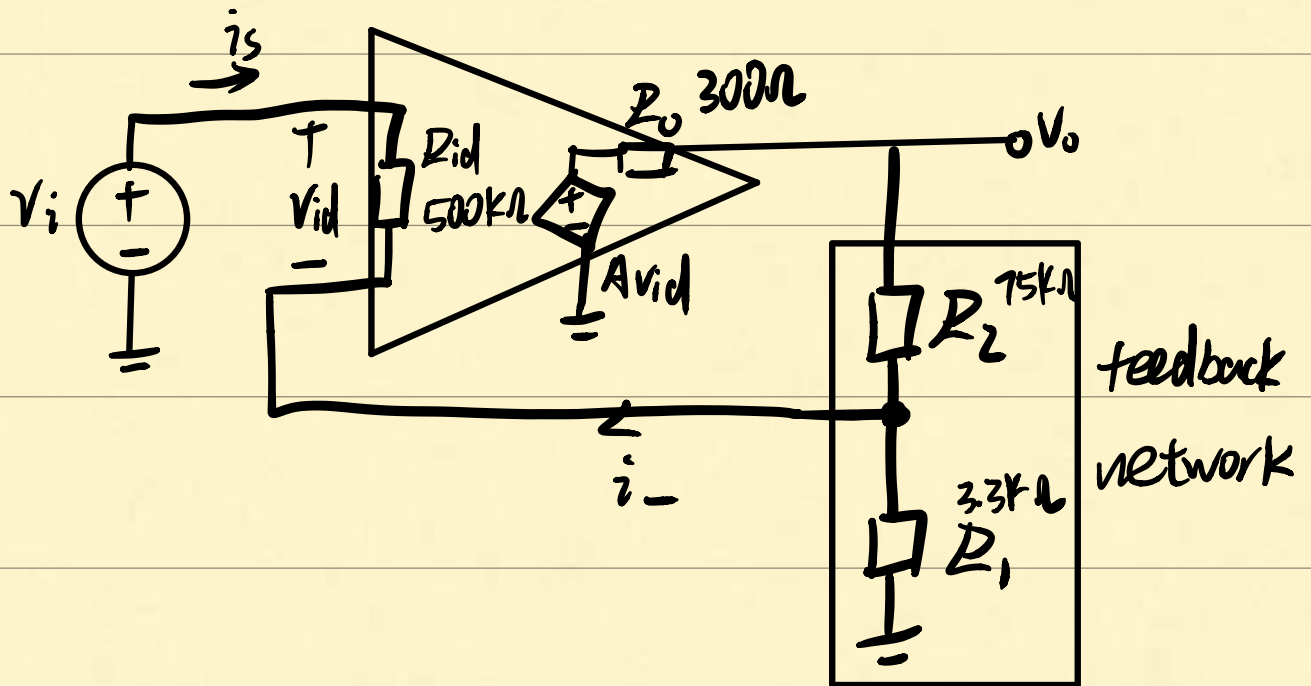Q4: A non-inverting amp is built using an op-amp with input resistance $R_{id} = 500\text{k}\Omega$ and output resistances $R_o = 300\Omega$. The resistances $R_1 = 33\text{k}\Omega$ $R_2 = 75\text{k}\Omega$



	Amp		
	Actual CL gain A_v	Input resistance R_{in}	Output resistance R_{out}
$A = 60\text{dB}$	23.18	$2.157 \times 10^7 \Omega$	6.953Ω
$A = 40\text{dB}$	19.18	$2.61 \times 10^6 \Omega$	57.526Ω

$$\text{feedback } \beta = \frac{R_1}{R_1 + R_2} = 0.0422$$

① when $A = 60 \text{ dB}$
 $= 10^{(\frac{60}{20})} = 1000$, $A_v^{\text{ideal}} = \frac{1}{\beta} = 1 + \frac{R_2}{R_1} = 23.73$

$$\text{loop gain } T = A\beta = 42.146$$

$$A_v^{\text{actual}} = A_v^{\text{ideal}} \cdot \left(\frac{T}{1+T} \right) = 23.18$$

$$R_{\text{in}} = R_{\text{id}}(1+T) = 2.157 \times 10^7 \Omega$$

$$R_{\text{out}} = \frac{R_o}{1+T} = 6.953 \Omega$$

② when $A = 40 \text{ dB}$
 $= 10^{(\frac{40}{20})} = 100$, $A_v^{\text{ideal}} = 23.73$

$$\text{loop gain } T = A\beta = 4.215$$

$$A_v^{\text{actual}} = A_v^{\text{ideal}} \left(\frac{T}{1+T} \right) = 19.18$$

$$R_{\text{in}} = R_{\text{id}}(1+T) = 2.61 \times 10^6 \Omega$$

$$R_{\text{out}} = \frac{R_o}{1+T} = 57.526 \Omega$$