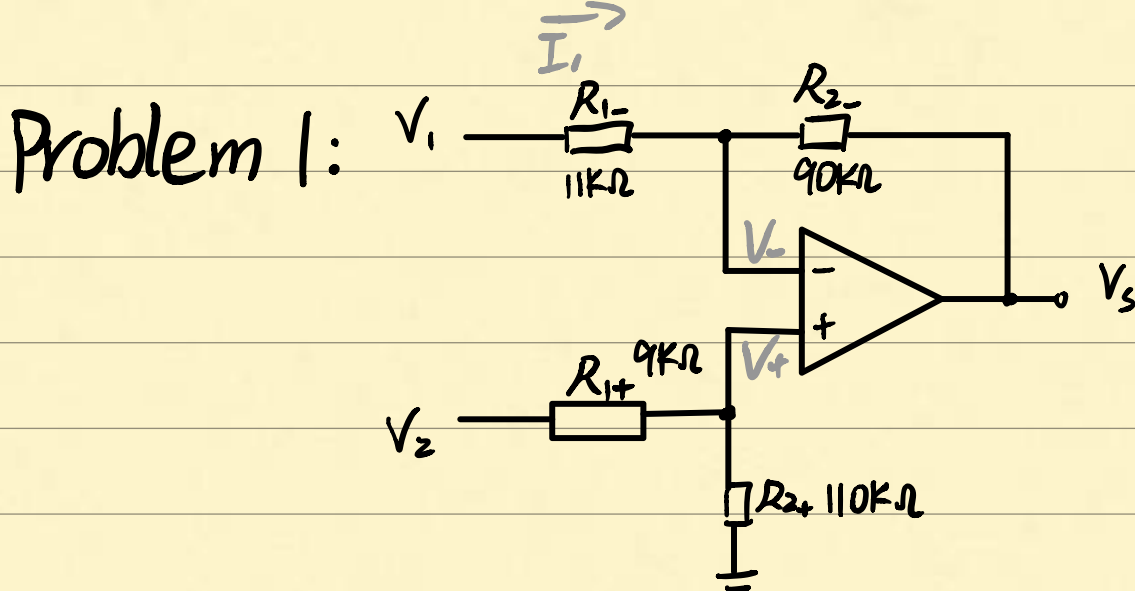




a) what are output Voltage V_s and common mode A_{cm} gain if the input voltage are $V_1 = 1V$ and $V_2 = 1V$?

$A_{cm} = 0.3058$	$V_s = 0.3058$
-------------------	----------------

$$V_+ = V_2 \cdot \frac{R_{2+}}{R_{1+} + R_{2+}} = 1 \cdot \frac{110K}{9K + 110K} = 0.9244V$$

$$V_- = V_+ = 0.9244V$$

$$I_{1-} = \frac{V_1 - V_-}{R_{1-}} = 6.873 \times 10^{-6} A, \quad I_+ = I_- = 0A = I_{2-}$$

$$V_s = V_- - I_{1-} \cdot R_{2-} = 0.3058V$$

$$A_{cm} = \frac{V_s}{\frac{V_1 + V_2}{2}} = 0.3058$$

b) What are the output voltage V_{out} and differential-mode A_{dm} gain if $V_1 = 0.5$, $V_2 = -0.5$

$$A_{dm} = -8.333$$

$$V_s = -8.333V$$

$$V_+ = V_2 \cdot \frac{R_{2+}}{R_{1+} + R_{2+}} = -0.5 \cdot \frac{110K}{4K + 110K} = -0.4622V$$

$$V_- = V_+ = -0.4622V$$

$$I_{L-} = \frac{V_1 - V_-}{R_{L-}} = \frac{0.4622V}{11K\Omega} = 8.75 \times 10^{-5}A$$

$$V_s = V_- - I_{L-} \cdot R_{2-} = -8.333V$$

$$A_{dm} = \frac{V_s}{V_1 - V_2} = -8.333$$

c) What is the common mode rejection ratio CMRR in dBs?

$$CMRR_{dB} = 28.7 \text{ dB}$$

$$CMRR = \frac{A_{dm}}{A_{cm}} = \left| \frac{-8.33}{0.306} \right| = 27.2$$

$$20 \lg |CMRR| = 28.7 \text{ dB}$$

d) Calculate output Voltage V_s if $V_1 = 1.05V$ and $V_2 = 0.95V$


$$V_s = -0.527V$$

$$V_s = (V_1 - V_2) \cdot A_{dm} + \frac{V_1 + V_2}{2} \cdot A_{cm}$$

$$= -0.833 + 0.306V$$

$$= -0.527V$$

Problem 2: Cascaded op-amps

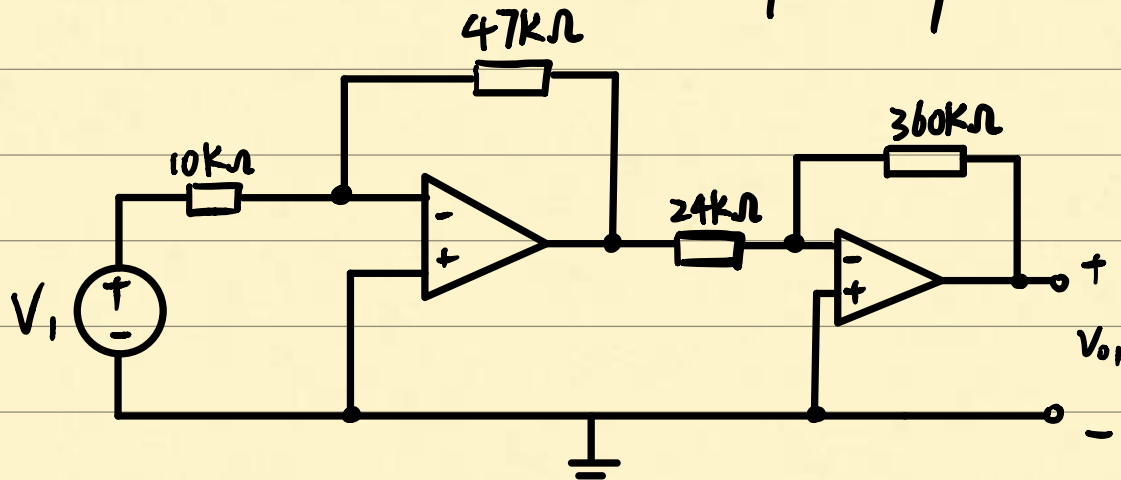

a) What are voltage gain A_v , and R_{in} , R_{out} ? ideal? ($A \rightarrow \infty$)

$A_v = 70.5$	$R_{in} = 10k\Omega$	$R_{out} = 0\Omega$
--------------	----------------------	---------------------

ideal: $R_{in} = 10k\Omega$

$$A_v = \left(-\frac{47k}{10k}\right) \cdot \left(-\frac{360k}{24k}\right) = 70.5$$

$$R_{out} = 0\Omega \text{ (ideal)}$$

b) What are A_v^{actual} , R_{in} , R_{out} when op-amps have $A = 10^4$ and op-amp $R_o = 200\Omega$

$A_v = 70.35$	$R_{in} = 10.005k\Omega$	$R_{out} = 0.3145$
---------------	--------------------------	--------------------

$$\beta_1 = \frac{10k}{10k + 47k} = 0.17544, \quad T_1 = A\beta_1 = 1754.4$$


$$\beta_2 = \frac{24k}{24k + 360k} = 0.0625, \quad T_2 = A\beta_2 = 625$$

$$A_v^{\text{actual}} = A_{v1} \cdot \frac{T_1}{1+T_1} \cdot A_{v2} \cdot \frac{T_2}{1+T_2} = 70.35$$

$$R_{in} = R_1 + \left(R_{id} \parallel \frac{R_2}{1+A}\right) = 10.005k\Omega$$

$$R_{out} = \frac{R_o}{(1+T_2)} = 0.3145\Omega$$

Problem 3:

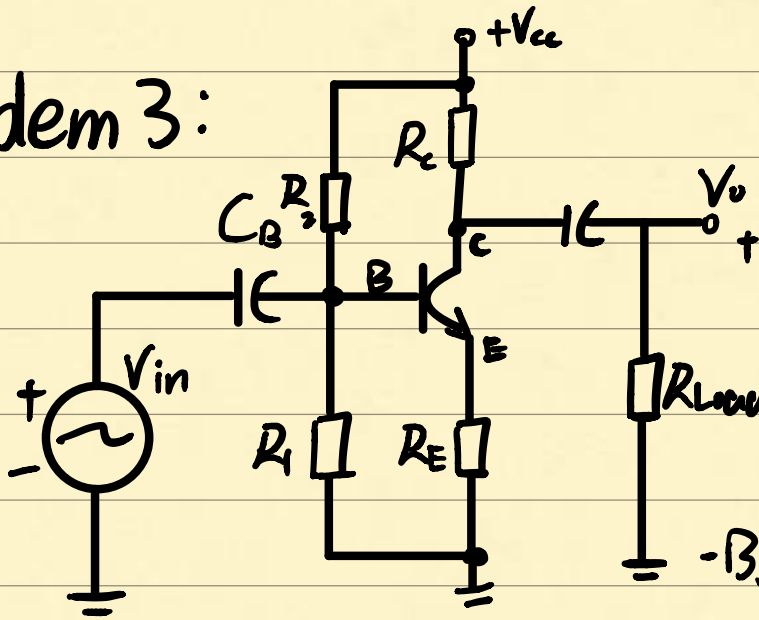

Ambient temperature
 $T = 300\text{K}$

$$V_{CC} = 16\text{V}, R_C = 2\text{k}\Omega$$

$$R_E = 0.75\text{k}\Omega$$

$$R_1 = 2\text{k}\Omega, R_2 = 8\text{k}\Omega$$

-BJT (NPN): $V_{BE} = 0.7\text{V}, \beta = 100$

$$V_A = 130\text{V}$$


$$r_e = \frac{26\text{mV}}{I_C} \quad r_o = \frac{V_A}{I_C}$$

a) operation point Q and r_e at 300K

$V_{CEQ} = 7.088\text{V}$	$I_{CQ} = 3.23\text{mA}$	$r_e = 8.045\Omega$
---------------------------	--------------------------	---------------------

at 300K, $r_e = \frac{26\text{mV}}{I_C}$
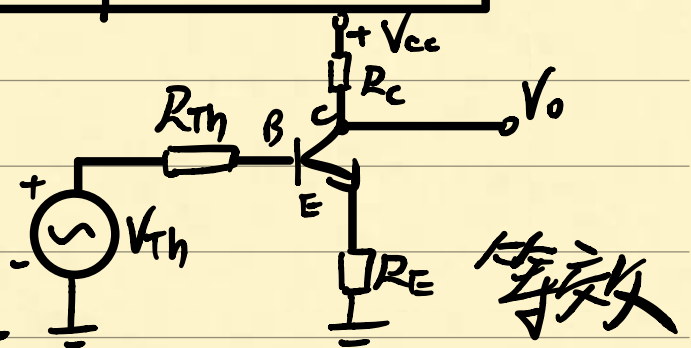
$$R_{Th} = R_1 // R_2 = \frac{1}{\frac{1}{2\text{k}} + \frac{1}{8\text{k}}} = 1.6\text{k}\Omega$$




$$V_{Th} = \frac{R_2}{R_1 + R_2} \cdot V_{CC} = \frac{2\text{k}}{2\text{k} + 8\text{k}} \cdot 16\text{V} = 3.2\text{V}$$

$$I_{BQ} = \frac{V_{Th} - 0.7}{R_{Th} + (1 + \beta)R_E} = 3.23 \times 10^{-5}\text{A}, I_{CQ} = \beta I_{BQ} = 3.23 \times 10^{-3}\text{A}$$

$$V_{CEQ} = V_{CC} - I_{CQ}R_C - I_{EQ}(1 + \beta)R_E = 7.088\text{V}$$

$$r_e = \frac{26\text{mV}}{I_C} = 8.045\Omega$$

b) no load:

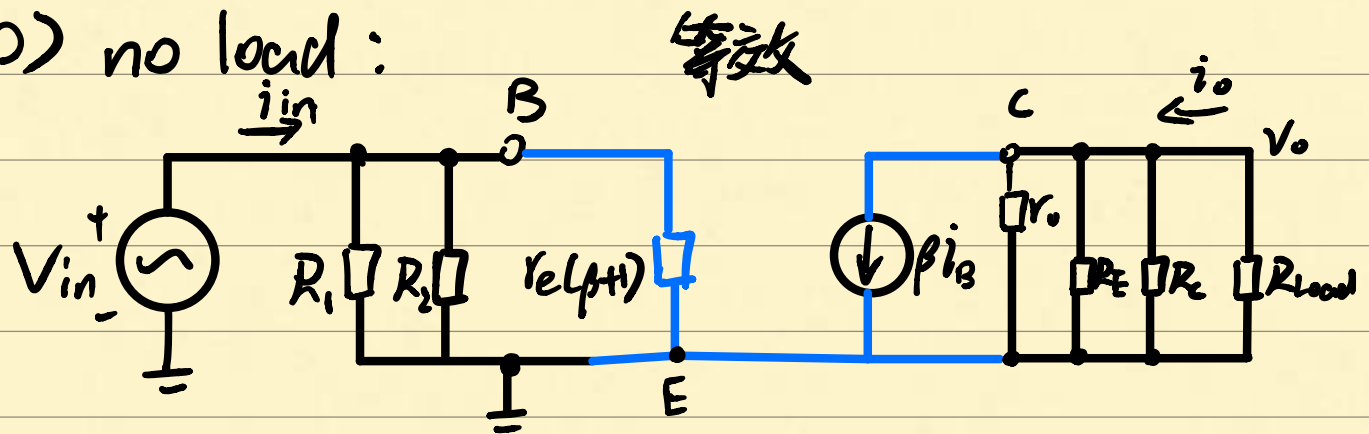

$R_{in} = 538.88 \Omega$	$R_{out} = 538.16 \Omega$	$A_v[\cdot] = -66.23$ (72)	$A_{v[dB]} = 36.42 \text{ dB}$
--------------------------	---------------------------	-------------------------------	--------------------------------

$$r_o = \frac{V_A}{I_C} = 40248 \Omega$$

$$R_{in} = R_1 // R_2 // r_e \cdot (1 + \beta) = 538.88 \Omega$$

$$R_{out} = r_o // R_E // R_C = 538.16 \Omega$$

$$A_{v_no\text{load}} = \frac{V_{out}}{V_{in}} = \frac{-\beta \cdot i_{in} \cdot R_{out}}{i_{in} \cdot r_e \cdot (1 + \beta)} = -66.23$$

$$A_{v_no\text{load_dB}} = 20 \lg |A_{v_no\text{load}}| = 36.42$$

C) with load: Known $i_{out} = 1 \cdot \sin(1000t) \text{ mA}$, $V_{in} = 100 \cdot \sin(1000 \cdot t) \text{ mV}$

$R_{load} [\text{k}\Omega]$	A_v		A_i		A_p	
	c.i.	$[\text{dB}]$	c.i.	$[\text{dB}]$	c.i.	$[\text{dB}]$
6.08	60.8	35.68 dB	5.388	14.63 dB	327.59	25.16 dB

$$i_{in} = \frac{V_{in}}{R_{in}} = 1.856 \times 10^{-4} \cdot \sin(1000 \cdot t)$$

$$V_{out} = i_{out} \cdot R_{out} + \overset{\text{(负载电压)}}{A_{v_no\text{load}}} \cdot V_{in} = (6.538 - 6.623) \sin(1000t) = -6.08 \cdot \sin(1000 \cdot t)$$

$$A_{v_load} = \frac{V_{out}}{V_{in}} = 60.8 \quad \dots \quad 35.68 \text{ dB}$$

$$A_i = \frac{i_{out}}{i_{in}} = 5.388 \quad \dots \quad 14.63 \text{ dB}$$

$$A_p = |A_{v_load}| \cdot |A_i| = 327.59 \quad \dots \quad 25.16 \text{ dB}$$

$$\star 10 \lg A_p =$$

$$R_{load} = \left| \frac{V_{out}}{I_{out}} \right| = 6.08 \text{ k}\Omega$$